

APPC, E & M: Unit B HW 5

Name: _____

Hr: ____ Due at beg of hr on: _____

UB, HW5, P1

Reference Video: "Review of Unit on DC Circuits (Part IV)"
 YouTube, lasseviren1, DC CIRCUITS playlist

Refer to the bridge-circuit diagrams at right to determine each of the following quantities. Put correct units on your answers.

SWITCH OPEN:

SWITCH CLOSED:

$$I_{4\Omega} =$$

$$I_{4\Omega} =$$

$$I_{8\Omega} =$$

$$I_{8\Omega} =$$

$$V_{4\Omega} =$$

$$V_{4\Omega} =$$

$$V_{8\Omega} =$$

$$V_{8\Omega} =$$

$$V_{3F} =$$

$$V_{3F} =$$

$$V_{6F} =$$


$$V_{6F} =$$

$$Q_{3F} =$$

$$Q_{3F} =$$

$$Q_{6F} =$$


$$Q_{6F} =$$

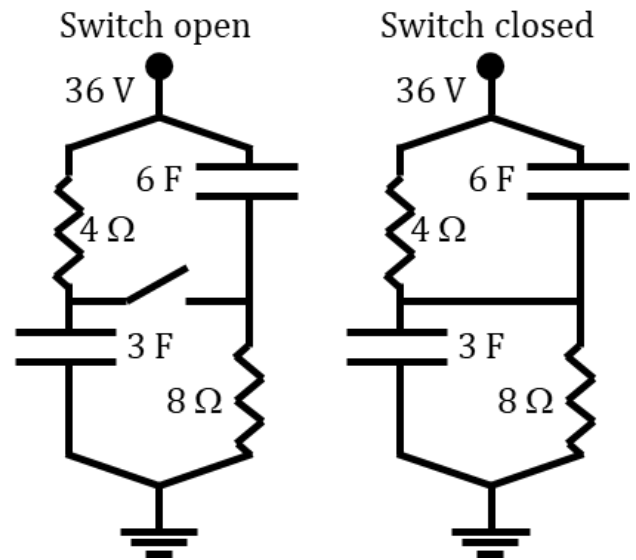

In this problem, we will begin to analyze the motion of an object of mass m that is dropped from rest in a fluid. (The fluid might be air, some other gas, or perhaps a liquid.) Let us suppose that the fluid will exert a drag force on the moving mass that is directly proportional to the speed of the mass, i.e., $|F_{drag}| = \beta v$.

- A. Assuming standard SI units, what must be the units on the constant β ?
- B. In the space above-right, draw a free-body diagram showing the forces acting as the mass falls.
- C. At some point during the fall, the mass will achieve terminal speed v_T . Derive an expression for the terminal speed v_T of the mass.
- D. Use your Part A answer to show that your Part C answer is dimensionally consistent.

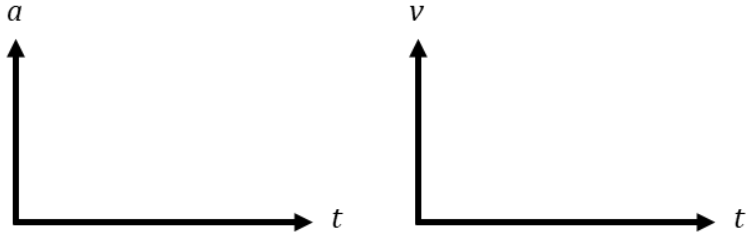E. In the two graphs shown, use a dashed line (- -) to sketch how the mass's acceleration a and speed v would vary with time if there were NO drag force from the fluid. Use a solid line to show how a and v will vary with time when there IS a drag force. Also, on the vertical axis of the appropriate graph, label the values g and v_T .



F. Using Newton's 2nd law, it is possible to write a differential equation that relates to this situation. Here, write – but do NOT solve – that differential equation.

UB, HW5, P3

Reference Video: "Objects Falling with Air Resistance (Part II)"


YouTube, lasseviren1, AIR RESISTANCE AND RC CIRCUITS playlist

This problem is a continuation of the previous one. Here, you will solve the differential equation you wrote in Part F of Problem 2.

- A. Solve your equation of Part F of Problem 2 for the term dt , i.e., $dt = ?$
Hint: First, divide through by m , then rearrange terms. On the right side of the equation, the denominator will look a bit unusual; namely, it will have multiple terms, one of which has ITS OWN denominator.
- B. We will need to integrate both sides, so re-write your Part A answer showing that you will integrate time from $t = 0$ to $t = t$ and that you will integrate velocity from $v = 0$ to $v = v$.
- C. Let's use u -substitution to solve your Part B equation. Write here what u should be set equal to; namely, the unusual-looking denominator mentioned in Part A.
- D. Now, differentiate your Part C answer with respect to v , i.e., find $du/dv = ?$
- E. Solve your Part D answer for dv .
- F. Substitute your answers to Parts C and E into your answer to Part B.
Be sure to include the same limits of integration mentioned in Part B.
- G. Here, do two steps in one: (1) Mentally integrate the LEFT side of your Part F answer (easy!) and (2) move all constants to the left side. Hint: This should leave you with only u -stuff to integrate on the right. Don't show the steps separately; show only one answer.
- H. Now, do two more steps in one: (1) Integrate the right side of your Part G answer and (2) un-substitute your Part C answer so that there aren't any more u terms, only v terms. Make sure to include the integration limits on the right side of the equation.
- I. Two MORE steps in one: (1) Substitute and evaluate the limits of integration on the right side and (2) use a law of logarithms to represent the limits as a quotient of terms, NOT as a difference.
- J. Rewrite your Part I answer, with one modification: On the right side, eliminate the large fraction line so that the thing in parentheses goes something like: " $1 - ???$ "
- K. All along, our goal has been to find an equation for the velocity of the dropped mass as a function of time, i.e., $v(t)$. At this point, in your Part J answer, there should be a v tucked inside some kind of logarithm function. Take the necessary step to "un-log" the v term. Remember, this must be done to both sides of your Part J answer.
- L. Solve your Part K answer for $v(t)$.
- M. Based on your Part L answer, write an expression for $a(t)$.


For RC circuits, the charge on the plates, the voltage across the plates, and the current in the circuit vary with time, i.e., these can be expressed as functions: $q(t)$, $V(t)$, and $i(t)$...all of which are exponential in format. In the graphs shown, draw approximate curves that represent how q , V , and i vary with time.

A. During charging...

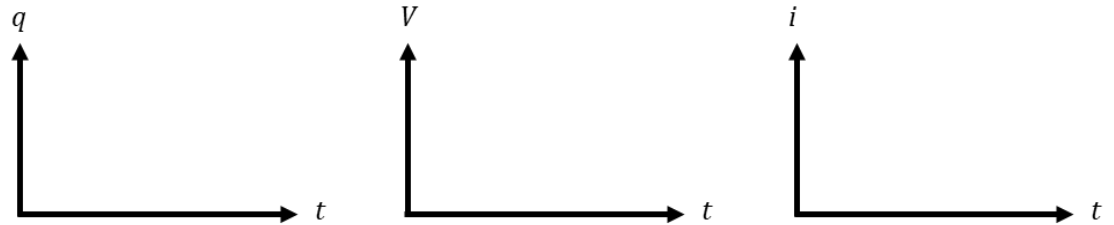

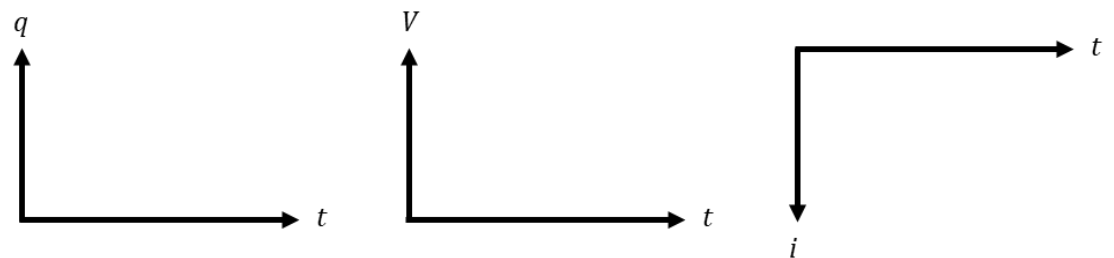B. During discharging...

Note that we will consider the current during discharge to have (-) values.



C. It has been observed that all graphs with an $e^{-?}$ term become asymptotically close to some final, constant value. If the asymptotic value is NOT equal to zero, we say it is a *climbing graph* (or *rising graph*), and the equation for such a graph has the term $(1 - e^{-?})$. If the asymptote IS zero, we say it is a *decaying graph* (or *falling graph*), and the equation for such a graph has merely the term $e^{-?}$. Below EACH graph in Parts A and B, write TWO of the following four labels:


$1 - e^{-?}$

decaying

$e^{-?}$

climbing

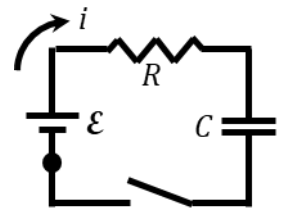Given: Here, you will derive an equation for $q(t)$ on the plates for a charging capacitor. With reference to the figure, starting at the dot, taking into account the assumed current i , and proceeding clockwise, the Kirchhoff's Loop Equation is: $\varepsilon - iR - V_c = 0$



A. Modify the given equation in two ways:

(1) change i to dq/dt and (2) change V_c to $\frac{q}{C}$.

B. What is it about your Part A answer that makes it a differential equation?

C. Now we will solve your differential equation. Rearrange your Part A answer so that the R and dt terms are the only ones on the left. The right side will look a little strange, in that it will have a fraction in the denominator.

D. We must integrate both sides, so re-write your Part C answer showing that you plan to integrate time from $t = 0$ to $t = t$ and charge from $q = 0$ to $q = q$.

E. We'll use *u-substitution* to solve your Part D equation. Write here what u should be set equal to; namely, the right-side denominator of your Part C answer.

F. Now, differentiate your Part E answer with respect to q , i.e., find $du/dq = ?$

G. Solve your Part F answer for dq .

H. Substitute your answers from Parts E and G into your answer to Part D. Be sure to include the same limits of integration mentioned in Part D.

I. Here, do two steps in one: (1) Mentally integrate the LEFT side of your Part H answer (easy!) and (2) move all constants to the left side. Hint: This should leave you with only u -stuff to integrate on the right. Don't show the steps separately; show only one answer.

J. Now, do two more steps in one: (1) Integrate the right side of your Part I answer and (2) un-substitute your Part E answer so that there aren't any more u terms, only q terms. Make sure to include the integration limits on the right side of the equation.

K. Two MORE steps in one: (1) Substitute and evaluate the limits of integration on the right side and (2) use a law of logarithms to represent the limits as a quotient of terms, NOT as a difference.

L. Rewrite your Part K answer, with one modification: On the right side, eliminate the large fraction line so that the thing in parentheses goes something like: "1 - ???"

M. At this point, in your Part L answer, there should be a q tucked inside some kind of logarithm function. Take the necessary step to "un-log" the q term.

N. Solve your Part M answer for $q(t)$.